

Name: Dalton McClair

Grade: /20

- 2) [20] The following truth table represents a Full Binary Adder. The two binary inputs are A and B and the carry from previous stage is Cin. The sum bit is S and the carry for the next stage is Cout.

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- 2.a) [2] Write the Boolean expression as a sum of Minterms:

$$\text{Sum} = f(A, B, \text{Cin}) = m_1 + m_2 + m_4 + m_5 = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C}$$

$$\text{Cout} = f(A, B, \text{Cin}) = m_3 + m_5 + m_6 + m_7 = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

- 2.b) [2] Optimize the above functions using K-maps:

$$\text{Sum} = f(A, B, \text{Cin}) = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} \quad \text{X0} \checkmark$$

$$\text{Cout} = f(A, B, \text{Cin}) = \bar{A}B + AC + BC \quad \text{X1} \checkmark$$

		BC			
		00	01	11	10
A	0		1		1
	1	1		1	

		BC			
		00	01	11	10
A	0			1	1
	1	1	1	1	1


cannot be optimized!

Name: Dalton McClain

Grade: /20

2.c) [2] Implement the above two optimized functions as a 3-input 2-output NOT-AND-OR network:

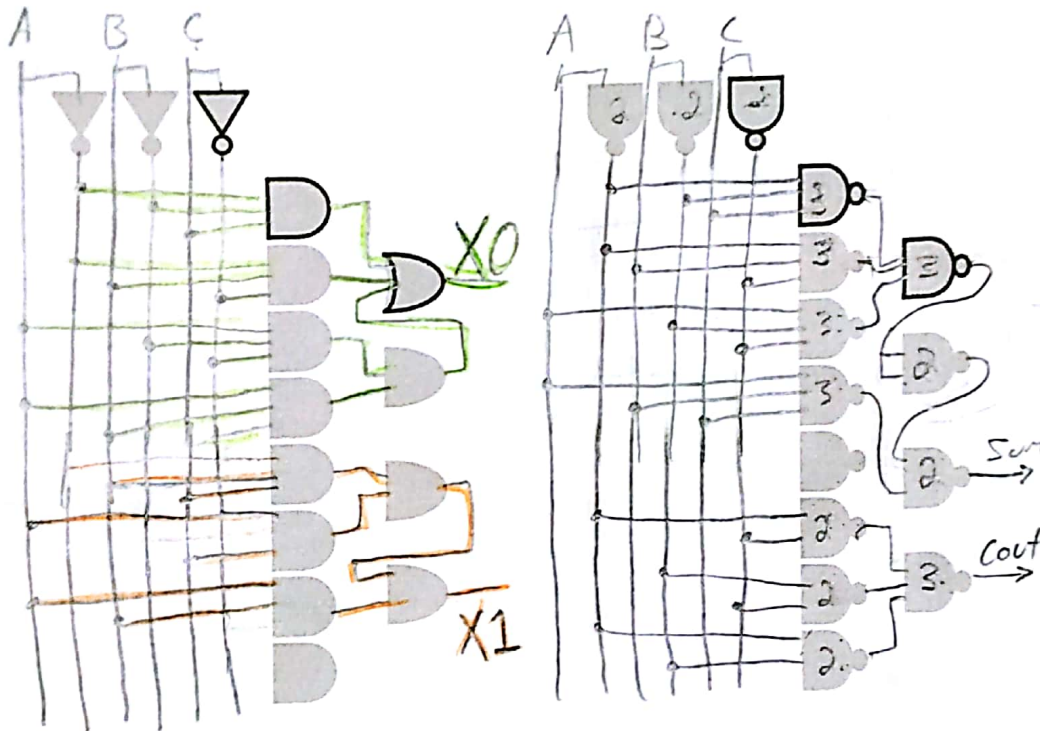2.d) [2] Convert the above network to all NAND gates:



2.e) [4] Build the above all-NAND circuit using the 7400 and 7410 logic chips (maximum 4 chips) on your breadboard and then connect it to your test platform to test it. Use 3 logic switches as inputs and 2 LEDs as outputs. You need to test all 8 different input combinations of the inputs.


Hint: Leave room on your breadboard for the 16-pin 74283.

2.f) [6] Connect your all-NAND 1-bit full adder to the standard 4-bit full adder (Chip 74283) making your adder the LSB of the 5-bit resulting adder. Use the following diagram to plan your wiring. To simplify the testing procedure, tie the two MSB bits to low level. Then, use 7 logic switches as inputs and 4 LEDs as outputs. To test your circuit, try as many input combinations as possible.


2.g) [2] You can verify the circuit design/behavior (the 5-bit adder) by implementing the circuit using Quartus. You may wish to do this before you actually build the circuit on the breadboard.

Name: Dalton McClary

Grade: /20

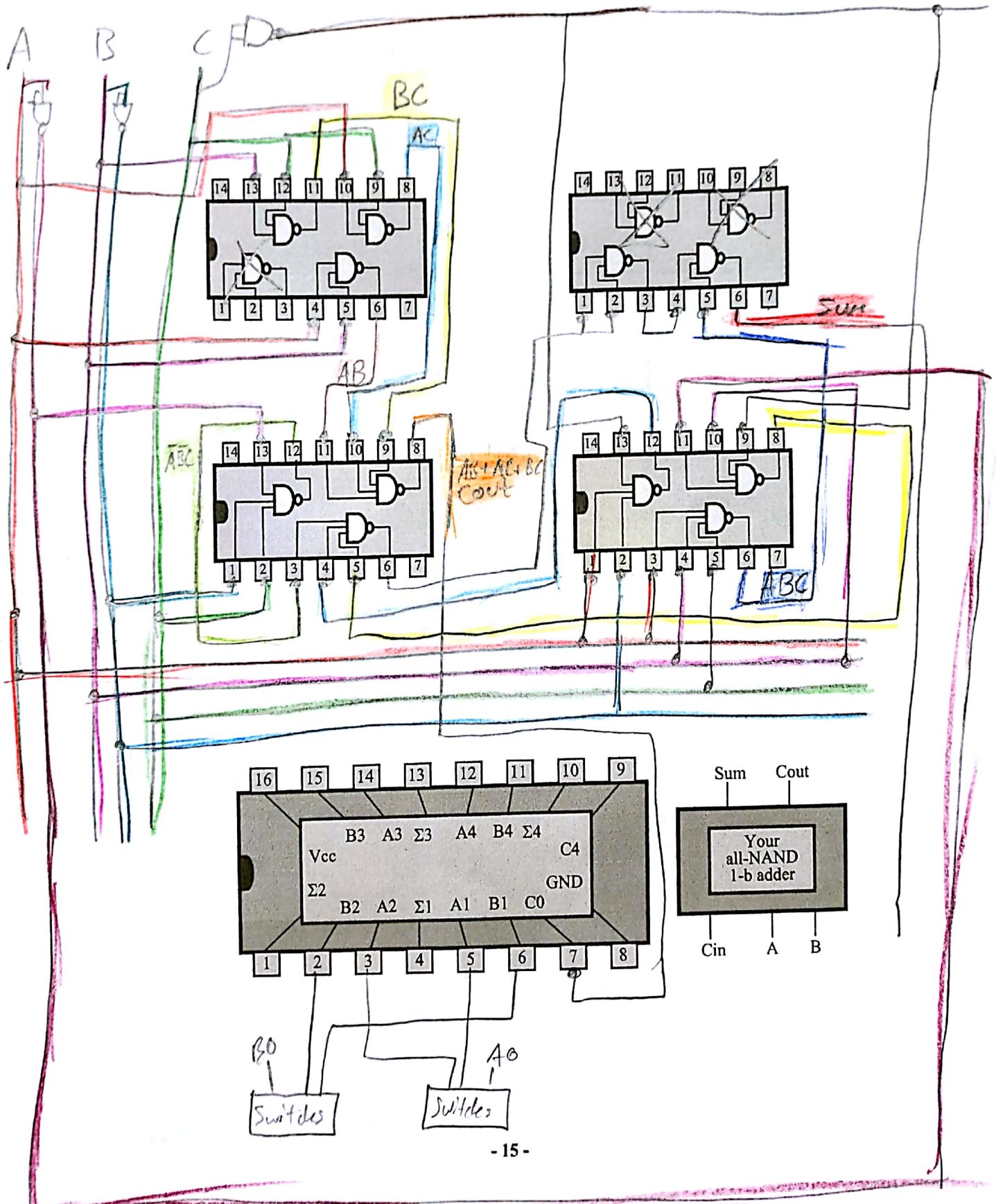


Dalton McClair
CDA 3201C Lab #2

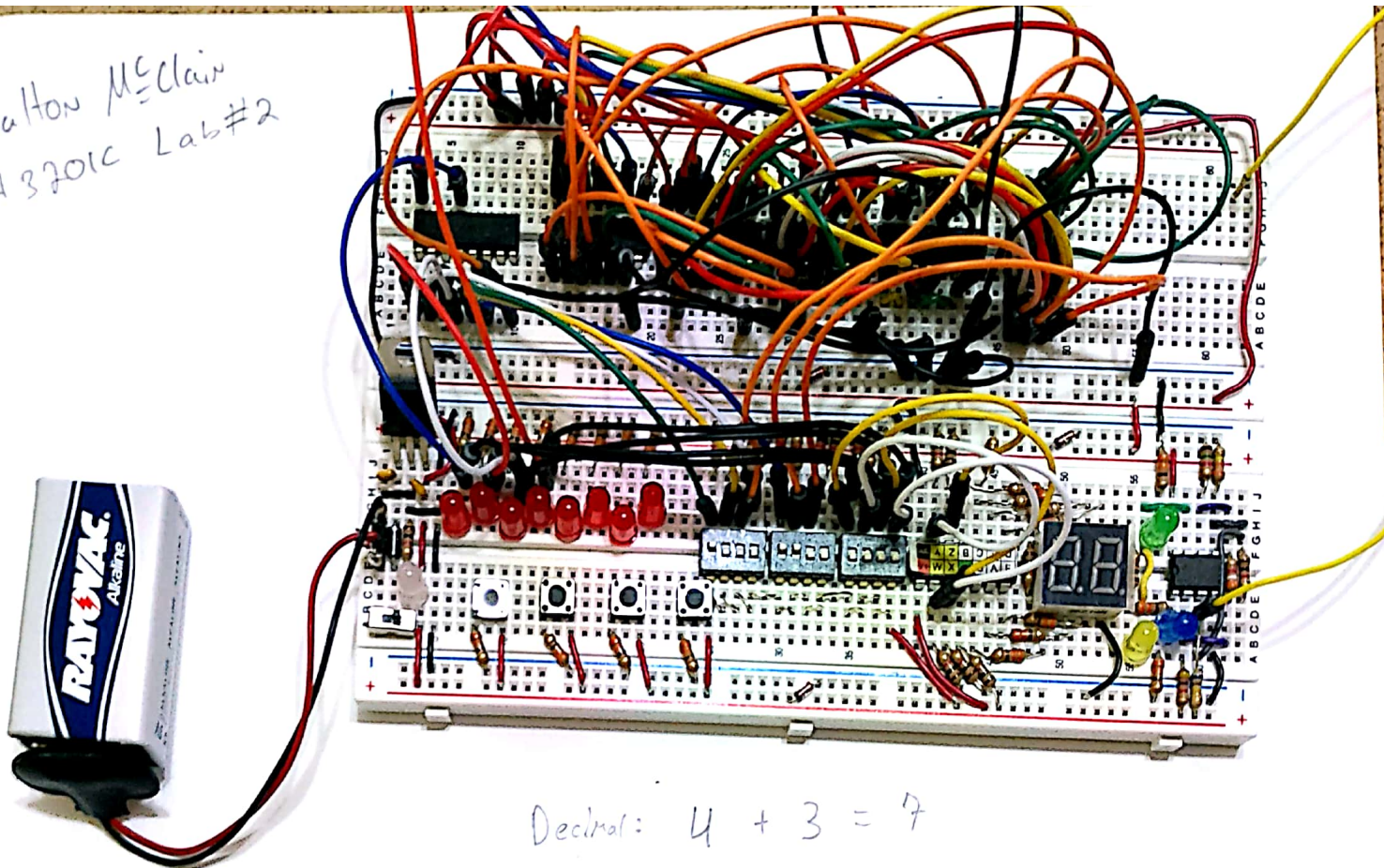

Decimal: $4 + 3 = 7$

Binary: $0100 + 0011 = 0111$

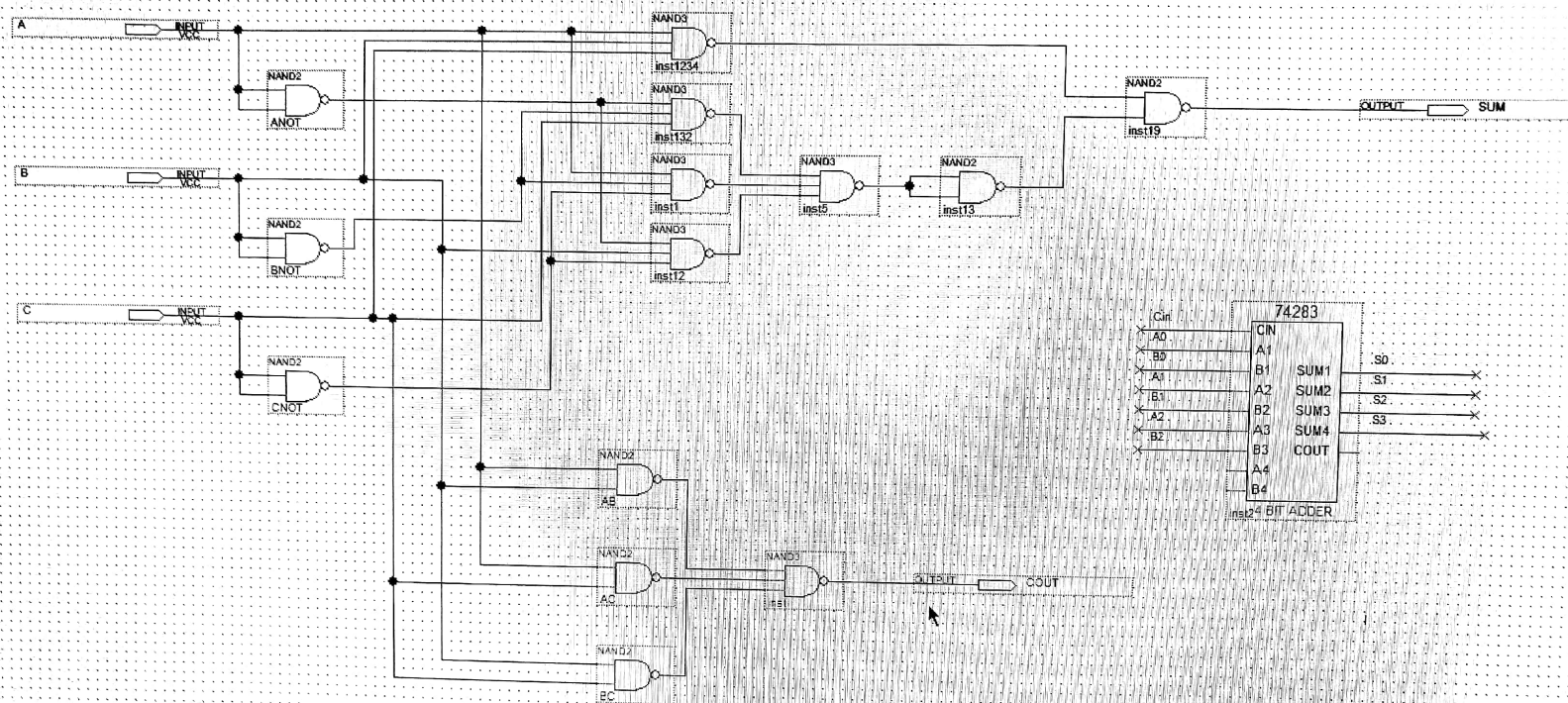

Compilation. Optimizations were skipped to reduce compilation time.

Output pin load capacitance assignment

Fully

Timing has not been

